


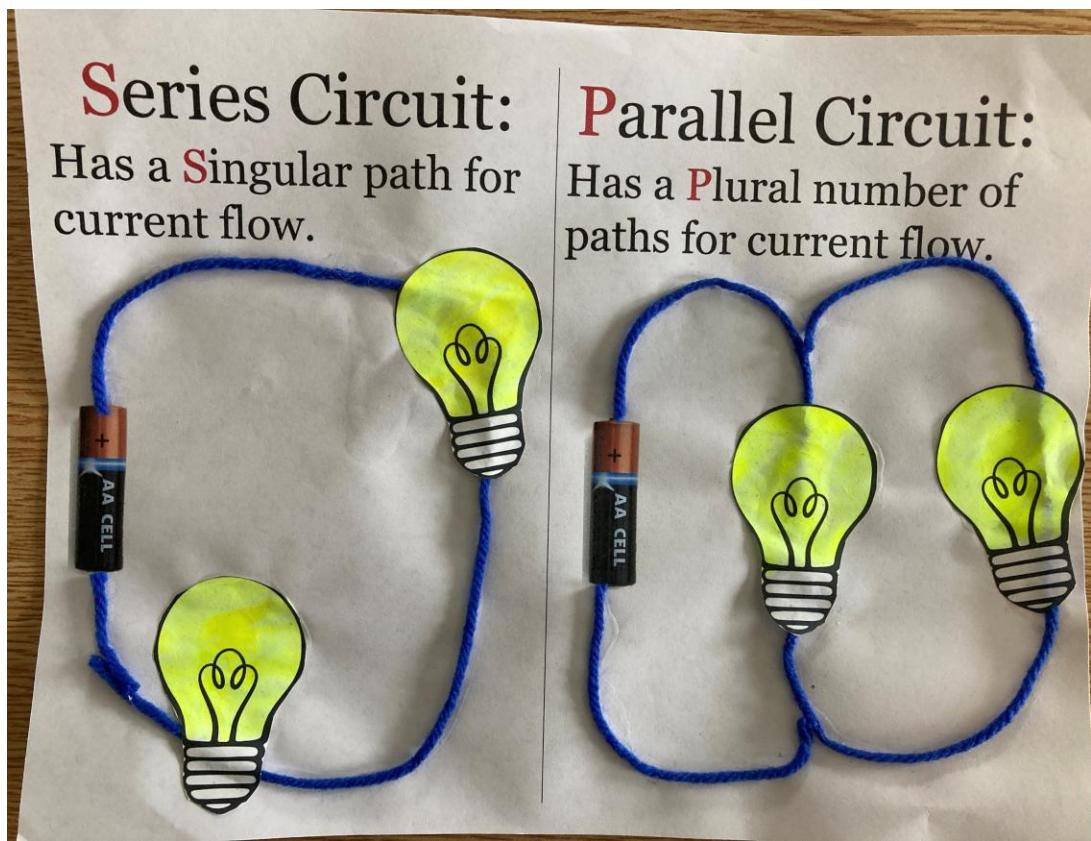
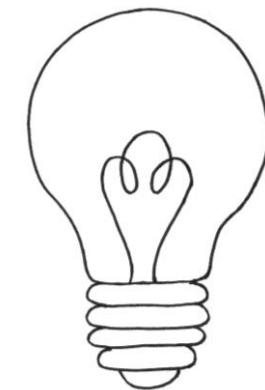
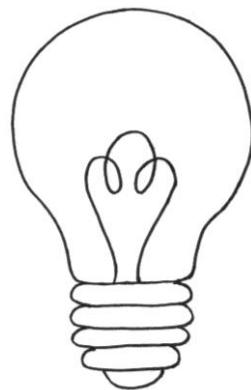


Series & Parallel Circuits

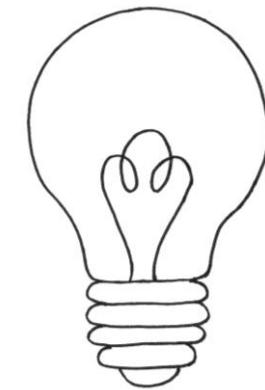

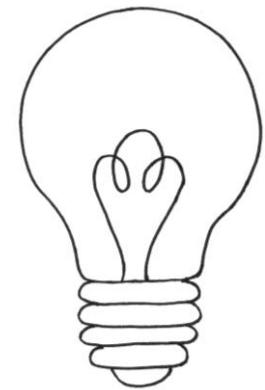- ❖ Color lightbulbs with highlighter and cut out
- ❖ Make the circuit paths with glue
- ❖ Place yarn on the glue
- ❖ Glue lightbulbs in place



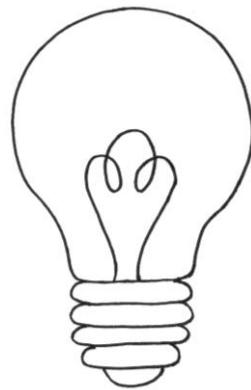

Series Circuit:

Has a **Singular** path for current flow.



Parallel Circuit:

Has a **Plural** number of paths for current flow.

